

Practice Quiz on Electronics

Name: _____ Date: _____

This is an informal quiz, but you may not consult your notes.

Identify the following circuit components:











6. What is Ohm's Law?

7. Draw a circuit diagram showing a battery, a resistor, and a capacitor all connected in parallel.

8. An interconnection of electronic components is called what?

9. What is a short circuit?

10. Draw the symbol for an AND gate.

11. Show the truth table for an OR gate.

12. How can you tell what the resistance of a resistor is?